

QP Code: D133839		Total Pages: 1	Name:
		Register No.	
THIRD SEMESTER UG DEGREE EXAMINATION, NOVEMBER 2025			
(CUFYUGP)			
ITY3CJ201 - DIGITAL ELECTRONICS			
2024 Admission onwards			
Maximum Time: 2 Hours		Maximum Marks: 70	
Section A			
All Questions can be answered. Each Question carries 3 marks (Ceiling: 24 Marks)			
1	Define 1's complement with an example.		
2	Convert $(458)_{10}$ to binary and hexadecimal.		
3	Perform binary subtraction: $(11010)_2 - (1011)_2$.		
4	Draw the logic symbol of XOR and write its truth table.		
5	State DeMorgan's Theorems.		
6	Write minterm and maxterm expressions for a two-variable function.		
7	What is a half adder? Draw its logic diagram.		
8	Differentiate multiplexer and demultiplexer.		
9	Write the truth table of SR flip flop.		
10	What is a shift register? Mention any two applications.		
Section B			
All Questions can be answered. Each Question carries 6 marks (Ceiling: 36 Marks)			
11	Explain binary multiplication with an example.		
12	Differentiate between BCD and ASCII codes with examples.		
13	Prove NAND gate as a universal gate.		
14	Simplify the Boolean expression $F(A,B,C)=A'B+AB'+ABC$ using Boolean algebra.		
15	Design a full adder using half adders.		
16	Explain the working of a BCD to 7-segment decoder.		
17	Explain JK flip flop with logic diagram and truth table.		
18	Distinguish between synchronous and asynchronous counters.		
Section C			
Answer any ONE. Each Question carries 10 marks (1x10=10 Marks)			
19	Explain different types of number system conversions with suitable examples.		
20	Design and explain a 4-bit shift register with block diagram.		