

D 92932

(Pages : 2)

Name.....

Reg. No.....

**THIRD SEMESTER (CBCSS—UG) DEGREE EXAMINATION
NOVEMBER 2020**

Electronics

ELE 3C 05—DIGITAL ELECTRONICS

Time : Two Hours

Maximum : 60 Marks

Section A

*Answer at least **eight** questions.*

Each question carries 3 marks.

All questions can be attended.

Overall Ceiling 24.

1. What do you mean by a bit and byte ?
2. How are negative numbers represented ?
3. What are the universal gates ? Why are they called so ?
4. What is a minterm ?
5. What is a half-adder ?
6. Why is a multiplexer called a data selector ?
7. What are the two types of flip-flops ?
8. What is the other name of asynchronous counter ? Why is that name ?
9. What are shift registers ?
10. What is a PROM ? Is it volatile ?
11. Explain the programming of ROM.
12. What are the two major disadvantages of EEPROM ?

(8 × 3 = 24 marks)

Turn over

Section B

*Answer at least **five** questions.*

Each question carries 5 marks.

All questions can be attended.

Overall Ceiling 25.

13. Discuss octal number system.
14. Prove that $AB + \bar{A}C + BC = AB + \bar{A}C$.
15. Realize a full subtractor.
16. Realize the logic expression using NAND gates only : $F_1 = \sum m (1, 3, 5, 8, 11, 12, 14, 15)$.
17. With neat diagrams, explain the working of a serial in, serial out shift register.
18. With neat diagrams, explain the operation of positive edge triggered JK flip-flop.
19. Explain in detail the different types of RAMs.

(5 × 5 = 25 marks)

Section C

*Answer any **one** question.*

The question carries 11 marks.

20. State and prove Boolean Algebra Laws.
21. Explain in detail a 4 bit asynchronous up counter.

(1 × 11 = 11 marks)