

138775

D 12010

(Pages : 2)

Name.....

Reg. No.....

THIRD SEMESTER (CBCSS—UG) DEGREE EXAMINATION  
NOVEMBER 2021

Electronics

ELE 3C 05—DIGITAL ELECTRONICS

(2019—2020 Admissions)

Time : Two Hours

Maximum : 60 Marks

Section A

Answer at least **eight** questions.

Each question carries 3 marks.

All questions can be attended.

Overall Ceiling 24.

1. What are alphanumeric codes ? For what they are used ?
2. What is 1' complement representation method ?
3. State and prove associative law of Boolean algebra.
4. What is a Maxterm ?
5. Can a multiplexer be used to realize logic functions ? If yes, in what ways this realization is better than realization using logic gates ?
6. What is an Encoder ?
7. What do you mean by toggling ?
8. What are the types of loading in a shift register ?
9. What are the asynchronous inputs of a flip-flop ?
10. List any four applications of counters.
11. What are RAMs ? How they differ from ROMs ?
12. Is ROM a volatile memory ? Explain.

(8 × 3 = 24 marks)

Turn over

138775

**Section B**

*Answer at least five questions.*

*Each question carries 5 marks.*

*All questions can be attended.*

*Overall Ceiling 25.*

13. Given  $A\bar{B} + \bar{A}B = C$ , show that  $A\bar{C} + \bar{A}C = B$ .
14. Discuss hexadecimal number system.
15. Realize the logic expression using MUX.  $F1 = \sum m(1, 3, 4, 7, 12, 14, 15)$ .
16. Realize a full adder using NAND gates only.
17. With neat diagrams, explain the working of 4-bit ring counter.
18. With neat diagrams, explain the operation of T and D flip-flops.
19. What are the different types of ROMs? Explain.

(5 × 5 = 25 marks)

**Section C**

*Answer any one question.*

*The question carries 11 marks.*

20. What are the different types of gates? Explain in detail each of them.
21. Design a 3 bit synchronous up counter.

(1 × 11 = 11 marks)